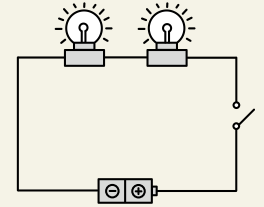


Spr
1

Topaz Science Knowledge Organiser

Energy: Electricity



How circuits are formed?

I can use symbols when drawing and labelling circuits accurately.

How does changing the voltage affect a circuit?

What happens when we add components to a circuit?

Can we design and test our own system?

Who was Thomas Edison?